

CEEN 3130
SWITCHING CIRCUITS THEORY

AUTHOR
Austin Koch

Vending Machine Simulation

PORTFOLIO PROJECT #2
Due May 6th, 2015

The Peter Kiewit Institute
University of Nebraska

Objectives

- To apply knowledge of VHDL and ASM state machines to a Real Life Problem
- To generate code that will function as a realistic Vending Machine

Design Requirements

Discussion of Constraints:

The purpose of this project is to generate code that will dispense out products based upon user inputs of various coins and selections. This project is an echo of many of the other projects and labs performed throughout the course. This project, though in aims to be a realistic model, will allow some leeway. First of which, the design does not accommodate for continuous inputs and would, in a real life setting, treat a prolonged input as an infinite sum of currency. This was accounted for by user monitored inputs.

The constraints of the project also included the necessity of a multiplexor in lieu of direct input selections, an Adder to attain the running total, a shift register to store that value, and a comparator to signify when enough change has been returned.

Components:

CONTROLLER:

The device uses a controller to input and output signals to and from the components in the lab.

ADDER:

This device asynchronously adds or subtracts two inputs, based upon whether or not a sub line is set high. In this case the storage register contents and the value selected by the mux.

COMPARATOR:

This component compares the value of the storage register with the value of the mux. If the storage is less than the arbitrary value, component will output a high signal indicating the total is too low to return change.

STORAGE REGISTER:

Takes on the value of sum of the Adder. Will store the incoming value if enable storage is high. Sends out stored value to be used by Adder.

System Operation

The machine will monitor to see if any change has been entered into the system, a nickel, dime, or quarter, and will keep a running total of the change deposited. Once the user makes a selection, then the machine will dispense the drink, subtract the cost from the running total, and then return change until there is nothing left in the running total. Change is signified by high outputs R5, R10, and R25, each signifying the value of the coin being changed. The device will signify when enough change has been given when the comparator deems the potential change value is greater than what is left on the store register.

The mux determines its values based on two select lines from the controller. The values change depending on state and will go through a cycle to test and see if using a quarter, dime, or nickel value is most appropriate.

After a price is selected the machine will go through each coin, starting with 25, and use the comparator to determine if the total is less than the change being subtracted. If it is, NEG will go high and the controller will turn off the arithmetic and move onto the next value. Once all three have been used, the total should be zero.

Portfolio Project 2 – Spring 2015.

CEEN 3130 Switching Circuit Theory

In this exercise you will design the electronics for a vending machine. The machine will accept nickels, dimes, and quarters. It has products that cost either 10 cents or 25 cents. It will give the correct change for the amount of money deposited and the product selected.

INPUTS: All inputs will be high for one clock period. They will not change at the same time as the rising edge of the clock. Inputs will be spaced so all of your machine's computations will be done before the next input occurs. You do not have to wait for the input to return to low before proceeding.

N: Nickel has been inserted

D: Dime has been inserted

Q: Quarter has been inserted

P10: Product costing 10 cents has been selected

P25: Product costing 25 cents has been selected

OUTPUTS:

R5: Returns a nickel. Is high for one clock period.

R10: Returns a dime. Is high for one clock period.

R25: Returns a quarter. Is high for one clock period.

OPERATION:

The machine will total the value of coins deposited. Your design does not have to limit the amount deposited. You can assume it will be less than 100.


When one of the product selectors is selected the value of the product is deducted from the total. The circuit will then return as many quarters as possible, followed by as many dimes as possible and finally nickels until the total is zero.

All the prior requirements for ASM charts, code, and simulations apply. Simulate using the three input sequences shown. As always, your simulation will have ALL signals into/out of the control unit, states, and values of counters and registers. Show the grouped values of the counters and registers.


The portfolio project will be submitted in hardcopy and electronic format. For the electronic format, all sections will be assembled into one pdf file with the *name yourlastname_proj2* and sent to Blackboard. (Don't zip the files together) Include the following verification.

I did not receive assistance in designing the circuit other than from the course instructor nor did I share my design with any other student.


Signed_____

 

 
Input: Quarter, Quarter, Dime, Nickel = 65; Selection = 10. Change: Quarter, Quarter, Nickel = 55.



 Input: Dime, Dime, Quarter, Nickel = 50; Selection = 10. Change: Quarter, Dime, Nickel = 40.



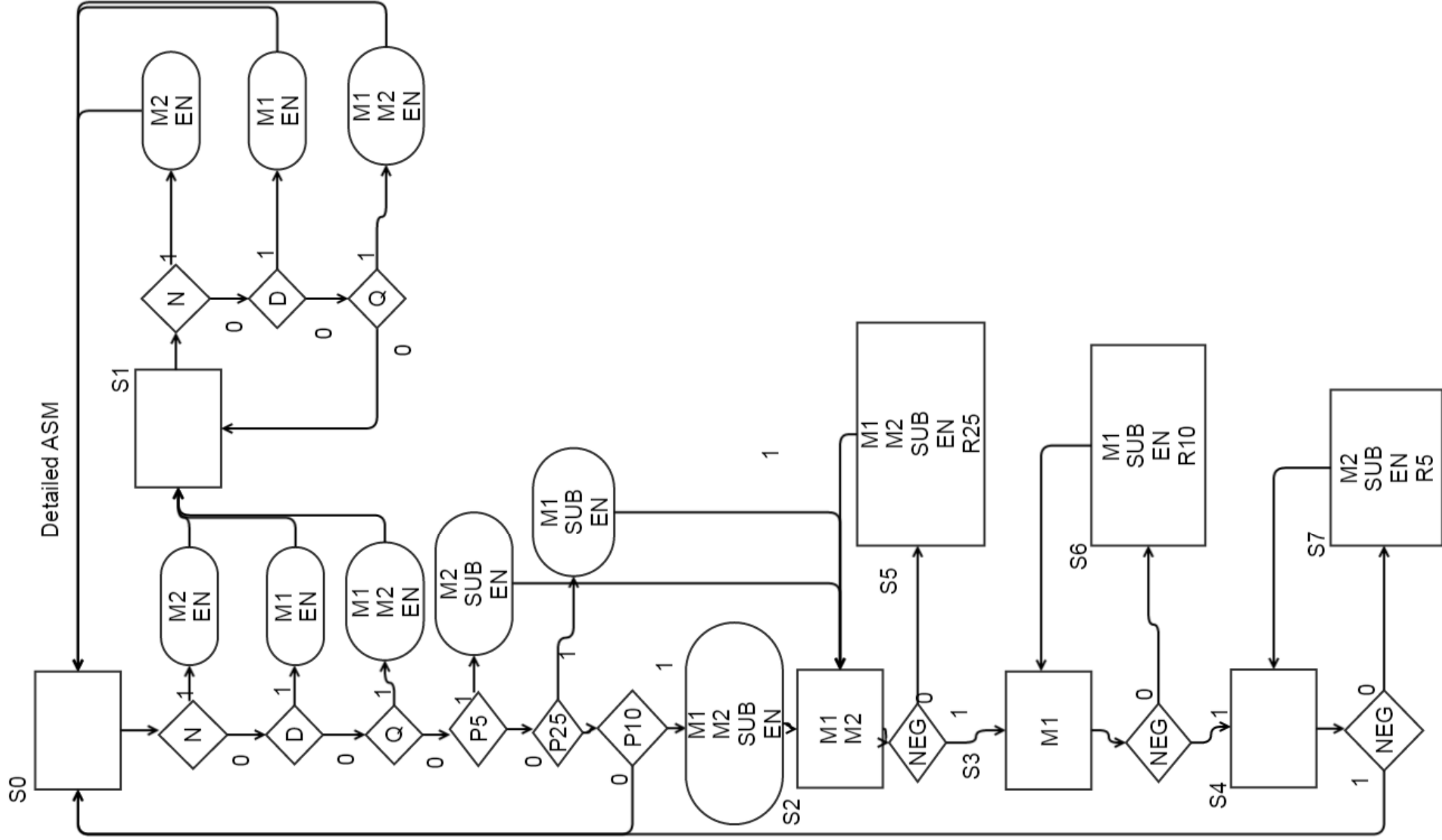Input: Dime, Nickel, Quarter = 40. Selection = 25. Change: Dime, Nickel = 15.



```
1  --Austin Koch 3130 Portfolio 2--
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.std_logic_unsigned.all;
5
6  entity addsub is
7      port(A, B : in std_logic_vector(7 downto 0);
8            S: in std_logic;
9            F : out std_logic_vector(7 downto 0));
10 end addsub;
11 architecture ADD_SUB of addsub is
12     begin
13         Process(A, B, S)
14         BEGIN
15             IF S = '1' THEN
16                 F <= A - B;
17             Else
18                 F <= A + B;
19             END IF;
20         END PROCESS;
21
22 end ADD_SUB;
23
24 -----
25
26 library ieee;
27 use ieee.std_logic_1164.all;
28 use ieee.std_logic_unsigned.all;
29
30 entity MUX is
31     port(S1, S2 : IN STD_LOGIC;
32           N, D, Q : IN std_logic_vector(7 downto 0);
33           F : out std_logic_vector(7 downto 0));
34
35 End MUX;
36
37 Architecture Behavior of MUX IS
38 --Signal Fs : STD_LOGIC_VECTOR(7 downto 0);
39 BEGIN
40
41     Process(N, D, Q, S1, S2)
42     BEGIN
43         IF S1 = '0' AND S2 = '0' THEN
44             F <= "00000000";
45         ElsIF S1 = '0' AND S2 = '1' THEN
46             F <= N;
47         ElsIF S1 = '1' AND S2 = '0' THEN
48             F <= D;
49         ELSE
50             F <= Q;
51         END IF;
52     END PROCESS;
53
54 END Behavior;
55
```



```
56 -----
57
58 LIBRARY ieee;
59 USE ieee.std_logic_1164.all;
60 USE ieee.std_logic_unsigned.all;
61
62 Entity Comp IS
63     PORT (A, B : IN STD_Logic_Vector(7 downto 0);
64           TH   : OUT STD_LOGIC);
65 END Comp;
66
67 Architecture Behavior OF Comp IS
68
69 BEGIN
70     Process (A, B)
71     BEGIN
72         TH <= '1';
73         IF A > B THEN
74             TH <= '0';
75         END IF;
76     END PROCESS;
77
78 END Behavior;
79
80 -----
81 library ieee;
82 use ieee.std_logic_1164.all;
83 use ieee.std_logic_unsigned.all;
84
85 entity STORE is
86     port(Reset, Clk, ENSTOR : IN STD_LOGIC;
87          D : in std_logic_vector(7 downto 0);
88          F : out std_logic_vector(7 downto 0));
89 END STORE;
90
91 ARCHITECTURE FUNC OF STORE IS
92 SIGNAL Fs : STD_LOGIC_VECTOR(7 downto 0);
93 BEGIN
94     PROCESS(Reset, CLK, ENSTOR, D, Fs)
95     BEGIN
96         IF RESET = '0' THEN
97             Fs <= "00000000";
98         ELSIF CLK'EVENT AND CLK = '1' AND ENSTOR = '1' THEN
99             Fs <= D;
100         ELSE
101             Fs <= Fs;
102         END IF;
103     END PROCESS;
104
105     F <= Fs;
106 END FUNC;
107 -----
108
109 library ieee;
110 use ieee.std_logic_1164.all;
```

```
111 use ieee.std_logic_unsigned.all;
112
113 ENTITY VEND IS
114     PORT( CLK, Resetn, N, D, Q, P5, P10, P25, NEG : IN STD_LOGIC;
115           M1, M2, SUB, R5, R10, R25, EN : OUT STD_LOGIC);
116 END VEND;
117
118 ARCHITECTURE BEHAVIOR OF VEND IS
119     TYPE State_type IS ( S0, S1, S2, S3, S4, S5, S6, S7);
120     SIGNAL y : State_type;
121 BEGIN
122     Process(CLK, RESETN, y)
123     BEGIN
124         IF RESETn = '0' THEN
125             y <= S0;
126         ELSIF CLK'EVENT AND CLK = '1' THEN
127             Case y IS
128                 WHEN S0 =>
129                     IF N = '1' OR D = '1' OR Q = '1' THEN
130                         y <= S1;
131                     ELSIF P5 = '1' OR P10 = '1' OR P25 = '1' THEN
132                         y <= S2;
133                     ELSE
134                         y <= S0;
135                     END IF;
136                 WHEN S1 =>
137                     IF N = '0' AND D = '0' AND Q = '0' THEN
138                         y <= S0;
139                     ELSE
140                         y <= S1;
141                     END IF;
142                 WHEN S2 =>
143                     IF NEG = '1' THEN
144                         y <= S3;
145                     ELSE
146                         y <= S5;
147                     END IF;
148                 WHEN S3 =>
149                     IF NEG = '1' THEN
150                         y <= S4;
151                     ELSE
152                         y <= S6;
153                     END IF;
154                 WHEN S4 =>
155                     IF NEG = '1' THEN
156                         y <= S0;
157                     ELSE
158                         y <= S7;
159                     END IF;
160                 WHEN S5 =>
161                     y <= S2;
162                 WHEN S6 =>
163                     y <= S3;
164                 WHEN S7 =>
165                     y <= S4;
```

```

166             WHEN OTHERS =>
167                 y <= S0;
168             END CASE;
169         END IF;
170     END PROCESS;
171
172
173     Process(y, P5, P10, P25, CLK, N, D, Q, NEG)
174     BEGIN
175         M1 <= '0';
176         M2 <= '0';
177         SUB <= '0';
178         EN <= '0';
179         R5 <= '0';
180         R10 <= '0';
181         R25 <= '0';
182
183
184         case y IS
185             WHEN S0 =>
186                 IF N = '1' THEN
187                     M2 <= '1';
188                     EN <= '1';
189                 ELSIF D = '1' THEN
190                     M1 <= '1';
191                     EN <= '1';
192                 ELSIF Q = '1' THEN
193                     M1 <= '1';
194                     M2 <= '1';
195                     EN <= '1';
196                 ELSIF P5 = '1' THEN
197                     SUB <= '1';
198                     M2 <= '1';
199                     EN <= '1';
200                 ELSIF P10 = '1' THEN
201                     SUB <= '1';
202                     M1 <= '1';
203                     EN <= '1';
204                 ELSIF P25 = '1' THEN
205                     SUB <= '1';
206                     M1 <= '1';
207                     M2 <= '1';
208                     EN <= '1';
209                 END IF;
210             WHEN S1 =>
211                 IF N = '1' THEN
212                     M2 <= '1';
213                     EN <= '1';
214                 ELSIF D = '1' THEN
215                     M1 <= '1';
216                     EN <= '1';
217                 ELSIF Q = '1' THEN
218                     M1 <= '1';
219                     M2 <= '1';
220                     EN <= '1';

```

```
221         END IF;
222     WHEN S2 =>
223         M1 <= '1';
224         M2 <= '1';
225     WHEN S3 =>
226         M1 <= '1';
227     WHEN S4 =>
228     WHEN S5 =>
229         M1 <= '1';
230         M2 <= '1';
231         SUB <= '1';
232         EN <= '1';
233         R25 <= '1';
234     WHEN S6 =>
235         M1 <= '1';
236         SUB <= '1';
237         EN <= '1';
238         R10 <= '1';
239     WHEN S7 =>
240         M2 <= '1';
241         SUB <= '1';
242         EN <= '1';
243         R5 <= '1';
244     END CASE;
245     END PROCESS;
246
247 END BEHAVIOR;
248
```

